



Design with Verilog 



Chap 6 – Introduction to HDL (d)



Credit to: MD Rizal Othman
Faculty of Electrical & Electronics Engineering
Universiti Malaysia Pahang

Ext: 6036

- Basic Unit – A module
- Module
 - Describes the functionality of the design
 - States the input and output ports
- Example: A Computer
 - Functionality: Perform user defined computations
 - I/O Ports: Keyboard, Mouse, Monitor, Printer

Module

- General definition


```
module module_name ( port_list );  
    port declarations;  
    ...  
    variable declaration;  
    ...  
    description of behavior  
endmodule
```

□ Example

```
module HalfAdder (A, B, Sum Carry);  
input A, B;  
output Sum, Carry;  
assign Sum = A ^ B;  
// ^ denotes XOR  
assign Carry = A & B;  
// & denotes AND  
endmodule
```

Dataflow

- **Dataflow:** Specify output signals in terms of input signals
- Example:
assign out = (sel & a) | (~sel & b);

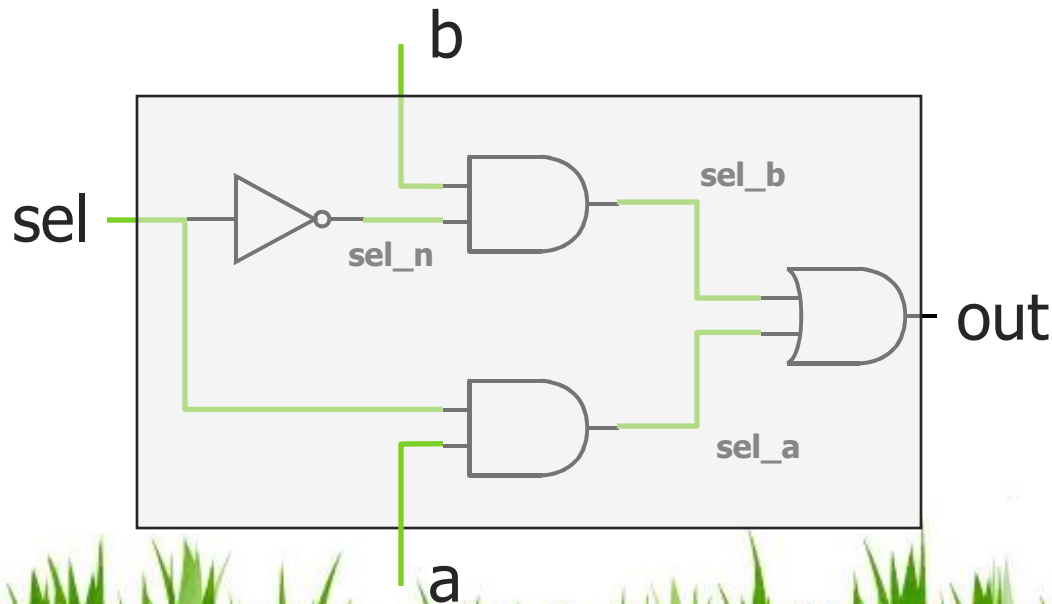

Dataflow Modeling

- Uses continuous assignment statement
 - Used to describe combinational logic
 - Output of the circuit evaluated whenever an input changes, i.e continuously assigned
 - Can be used ONLY for nets, NOT for register variables
 - Format: **assign** [delay] net = expression;
 - Example: **assign** sum = a ^ b;
- **Delay**: Time duration between assignment from RHS to LHS
- All continuous assignment statements execute concurrently
- Order of the statement does not impact the design

Dataflow Modeling (cont.)

- Delay can be introduced
 - Example: `assign #2 sum = a ^ b;`
 - “#2” indicates 2 time-units
- Associate time-unit with physical time
 - ``timescale` time-unit/time-precision
 - Example: ``timescale 1ns/100 ps`
- Timescale
 - ``timescale 1ns/100ps`
 - 1 Time unit = 1 ns
 - Time precision is 100ps (0.1 ns)
 - 10.512ns is interpreted as 10.5ns

Dataflow Modeling (cont.)

- Restrictions on Data Types:
 - Can use only *wire* data type
 - Cannot use *reg* data type

- Example:

```
`timescale 1ns/100ps
module HalfAdder (A, B, Sum, Carry);
    input A, B;
    output Sum, Carry;
    assign #3 Sum = A ^ B;
    assign #6 Carry = A & B;
endmodule
```

Dataflow Modeling (cont.)



1. Implementation of a 2x4 decoder.

```
module decoder_2x4 (out, in0, in1);
```

```
output out[0:3];
```

```
input in0, in1;
```

```
// Data flow modeling uses logic operators.
```

```
assign out[0:3] = { ~in0 & ~in1, in0 & ~in1, ~in0 & in1, in0 & in1 };
```

```
endmodule
```

2. Implementation of a Full adder.

```
module full_adder (sum, c_out, in0, in1, c_in);
```

```
output sum, c_out;
```

```
input in0, in1, c_in;
```

```
assign { c_out, sum } = in0 + in1 + c_in;
```

```
endmodule
```

Behavioral Modeling

- **Behavioral:** Algorithmically specify the behavior of the design

- Example:

```
if (select == 0) begin
```


```
    out = b;
```

```
end
```

```
else if (select == 1) begin
```

```
    out = a;
```

```
end
```

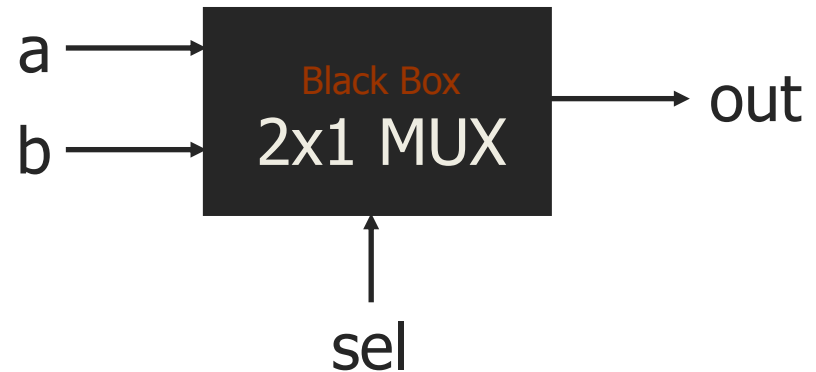

2. Behavioral Modeling

- Behavioral modeling is used to describe complex circuits.
- It is primarily used to model sequential circuits, but can also be used to model pure combinatorial circuits.
- The behavior of the design is described using procedural constructs: initial Statements and always Statements

Behavioral Modeling (cont.)

- **always** statement : Sequential Block
 - Sequential Block: All statements within the block are executed sequentially
- When is it executed?
 - Occurrence of an event in the sensitivity list
 - Event: Change in the logical value
- Statements with a Sequential Block: Procedural Assignments
 - can drive only **reg data type**.
 - Which means left-side data (output) type cannot be nets.
 - Can occur only within an initial or an always statement.
 - It can model both combinational and sequential logic.

Behavioral Modeling (cont.)

- **Example:**

```
module mux_2x1(a, b, sel, out);
```

```
  input a, a, sel;
```

```
  output reg out;
```

```
  always @(a or b or sel)
```

```
  begin
```

```
    if (sel == 1)
```

```
      out = a;
```

```
    else out = b;
```

```
  end
```

```
endmodule
```

Sensitivity List

Behavioral Modeling (cont.)

- Delay in Procedural Assignments
 - Inter-Statement Delay
 - Intra-Statement Delay
- Inter-Assignment Delay
 - Example:
Sum = A ^ B;
#2 Carry = A & B;
 - Delayed execution
- Intra-Assignment Delay
 - Example:
Sum = A ^ B;
Carry = #2 A & B;
 - Delayed assignment

Procedural Statement

- Two Procedural Statement
 - **initial** Statement
 - **always** Statement
- **initial** Statement : Executes only once
- **always** Statement : Executes in a loop
- Example:

```
...  
initial begin  
    Sum = 0;  
    Carry = 0;  
end  
...
```

```
...  
always @(A or B) begin  
    Sum = A ^ B;  
    Carry = A & B;  
end  
...
```


Event Control

- Event Control
 - Edge Triggered Event Control
 - Level Triggered Event Control
- Edge Triggered Event Control
 - @ (posedge CLK) //Positive Edge of CLK
 - Curr_State = Next_state;

@ negedge	@ posedge
1 → x	0 → x
1 → z	0 → z
1 → 0	0 → 1
x → 0	x → 1
z → 0	z → 1

- Level Triggered Event Control
 - @ (A or B) //change in values of A or B
 - Out = A & B;

```
module cont_proc (in1, in2, out1_cont, out2_cont, out1_proc, out2_proc);
input in1, in2;
output out1_cont, out2_cont, out1_proc, out2_proc;

wire in1, in2 ,out1_cont, out2_cont;
reg out1_proc, out2_proc;
//continuous assignment
assign #2 out1_cont = in1 | in2;
assign #1 out2_cont = in1 | in2;

always@(in1, in2) begin
//procedural assignment
#2 out1_proc = in1 | in2;
#1 out2_proc = in1 | in2;
end
endmodule
```

Loop Statements

- Loop Statements
 - Repeat
 - While
 - For
- Repeat Loop
 - Example:
 - `repeat (Count)`
 - `sum = sum + 5;`
 - If condition is a `x` or `z` it is treated as 0

Loop Statements (cont.)

- While Loop

- Example:

- ```
while (Count < 10) begin
```

- ```
    sum = sum + 5;
```

- ```
 Count = Count + 1;
```

- ```
end
```

- If condition is a **x** or **z** it is treated as 0

- For Loop

- Example:

- ```
for (Count = 0; Count < 10; Count = Count + 1) begin
```

- ```
    sum = sum + 5;
```

- ```
end
```

# Conditional Statements

- **if** Statement
- Format:
  - if** (condition)  
    procedural\_statement
  - else if** (condition)  
    procedural\_statement
  - else**  
    procedural\_statement
- Example:
  - if** (Clk)  
    Q = 0;
  - else**  
    Q = D;

# Conditional Statements (cont.)

- Case Statement
- Example 1:

`case (X)`

`2'b00: Y = A + B;`

`2'b01: Y = A - B;`

`2'b10: Y = A / B;`

`endcase`

# Conditional Statements (cont.)

- Variants of **case** Statements:
  - **casex** and **casez**
- **casez** – z is considered as a don't care
- **casex** – both x and z are considered as don't cares
- Example:  
**casez** (X)  
    2'b1z: A = B + C;  
    2'b11: A = B / C;  
**endcase**





## ***1. Implementation of a full adder.***

```
module full_adder (sum, c_out, in0, in1, c_in);
```

```
output sum, c_out;
```

```
reg sum, c_out
```

```
input in0, in1, c_in;
```

```
always @(in0, in1, c_in)
```

```
{c_out, sum} = in0 + in1 + c_in;
```

```
endmodule
```

## ***2. Implementation of a 8-bit binary counter.***

```
module (count, reset, clk);

output [7:0] count;
reg [7:0] count;

input reset, clk;

// consider reset as active low signal

always @(posedge clk, negedge reset)
begin
if(reset == 1'b0)
count <= 8'h00;
else
count <= count + 8'h01;
end

endmodule
```

- ***Implementation of a Full adder using Dataflow modeling***

```
module full_adder (sum, c_out,
in0, in1, c_in);
```

```
output sum, c_out;
input in0, in1, c_in;
```

```
assign { c_out, sum } = in0 + in1 +
c_in;
```

```
endmodule
```

- ***Implementation of a full adder using Behavioral modeling***

```
module full_adder (sum, c_out,
in0, in1, c_in);
```

```
output sum, c_out;
reg sum, c_out
```

```
input in0, in1, c_in;
```

```
always @(*)
{c_out, sum} = in0 + in1 + c_in;
```

```
endmodule
```

## ***3. Implementation of a 4x1 multiplexer using Dataflow and Behavioral modeling.***

Module...

....

....

....

endmodule



# 3. Structural Modeling

---

## 1. Data flow:

- To design combinational ONLY
- Use *assign* statement

## 2. Behavior

- To design combinational and sequential circuits
- Uses arithmetic expressions, procedural assignments (*initial* and *always* ), or other Verilog control flow structures



### 3. Structural Modeling


---

- A top-down design by combining lower-level logic modules into a larger structural module.
- Each lower-level modules (sub-modules) must have previously compiled and tested for correct functional operation
- Structural modeling can be described using build-in gate primitives or module instances in any combination
- Interconnections between instances are specified using nets
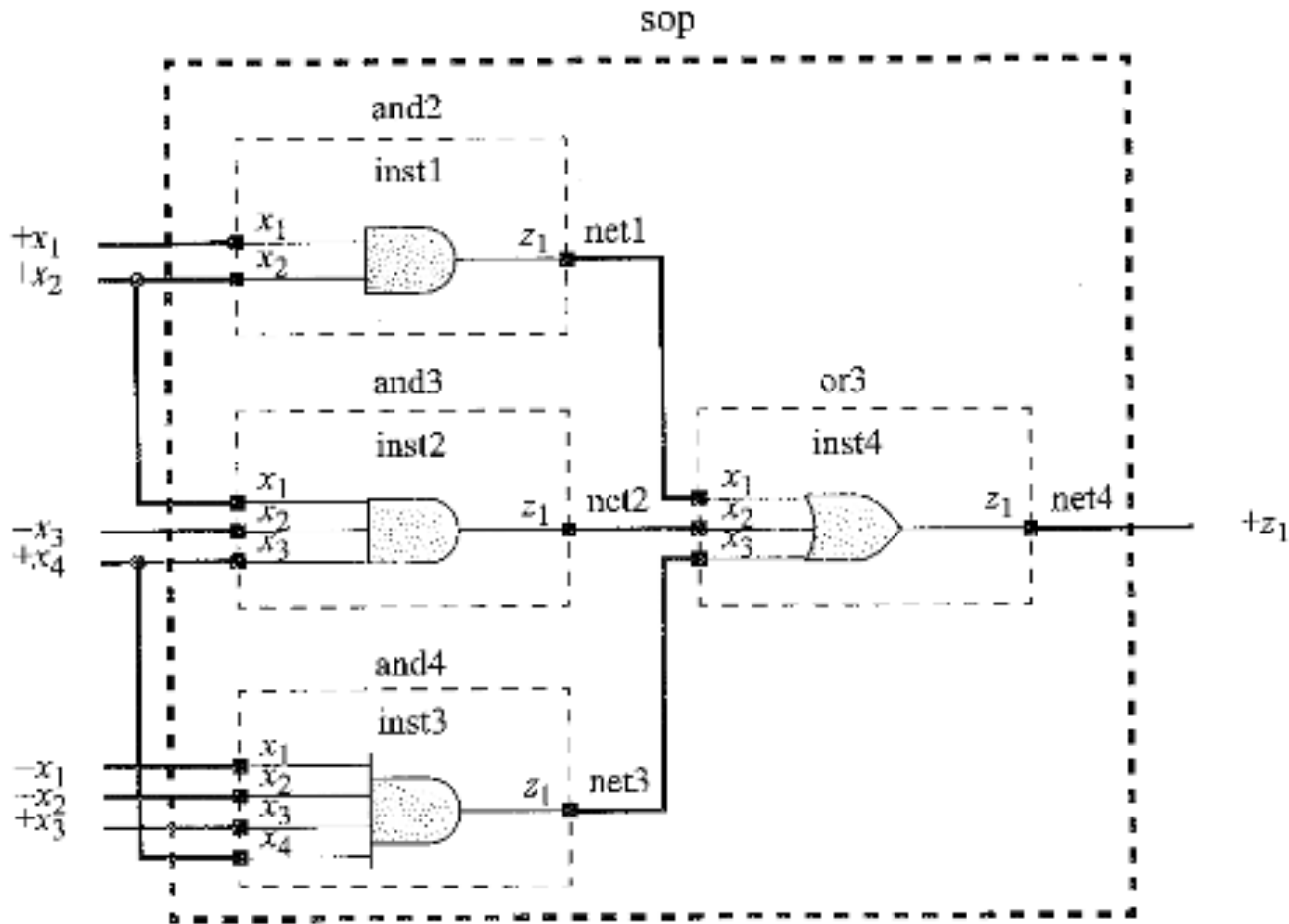
### 3. Structural Modeling (Example...)

Design the circuit based on expression:

$$z_1 = x_1x_2 + x_2x_3'x_4 + x_1'x_2'x_3x_4$$







 
### 3. Structural Modeling (Example...)

Design a full adder circuit using structural modeling




$$sum = a \oplus b \oplus cin$$

$$cout = cin(a \oplus b) + ab$$

$$sum = a \oplus b$$

$$cout = ab$$

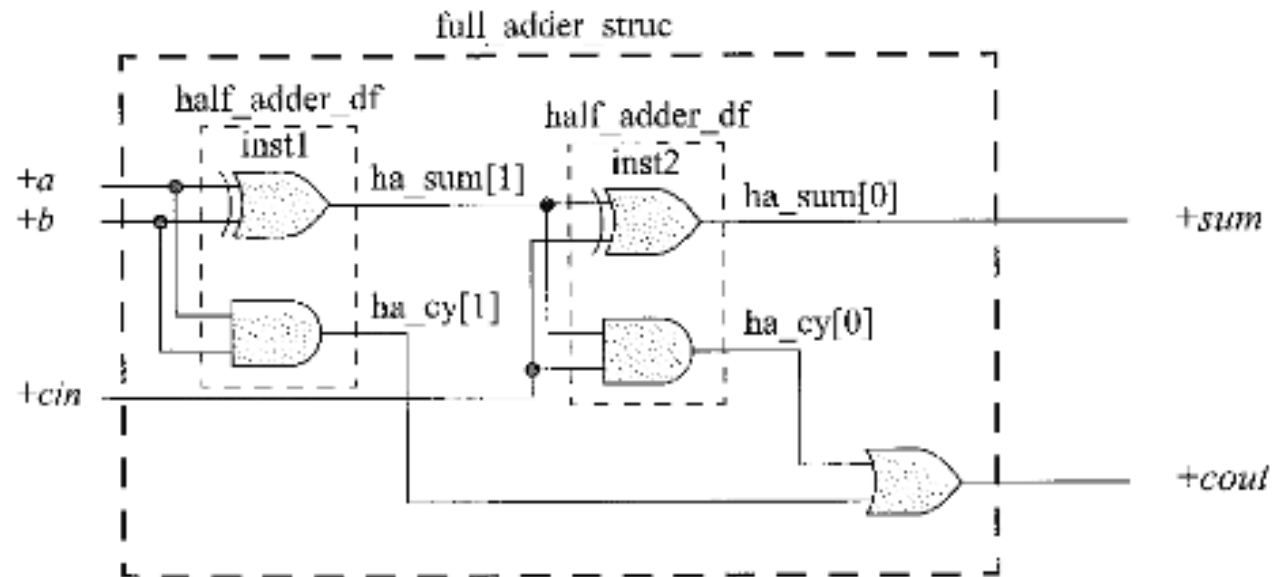


# Group discussion

---


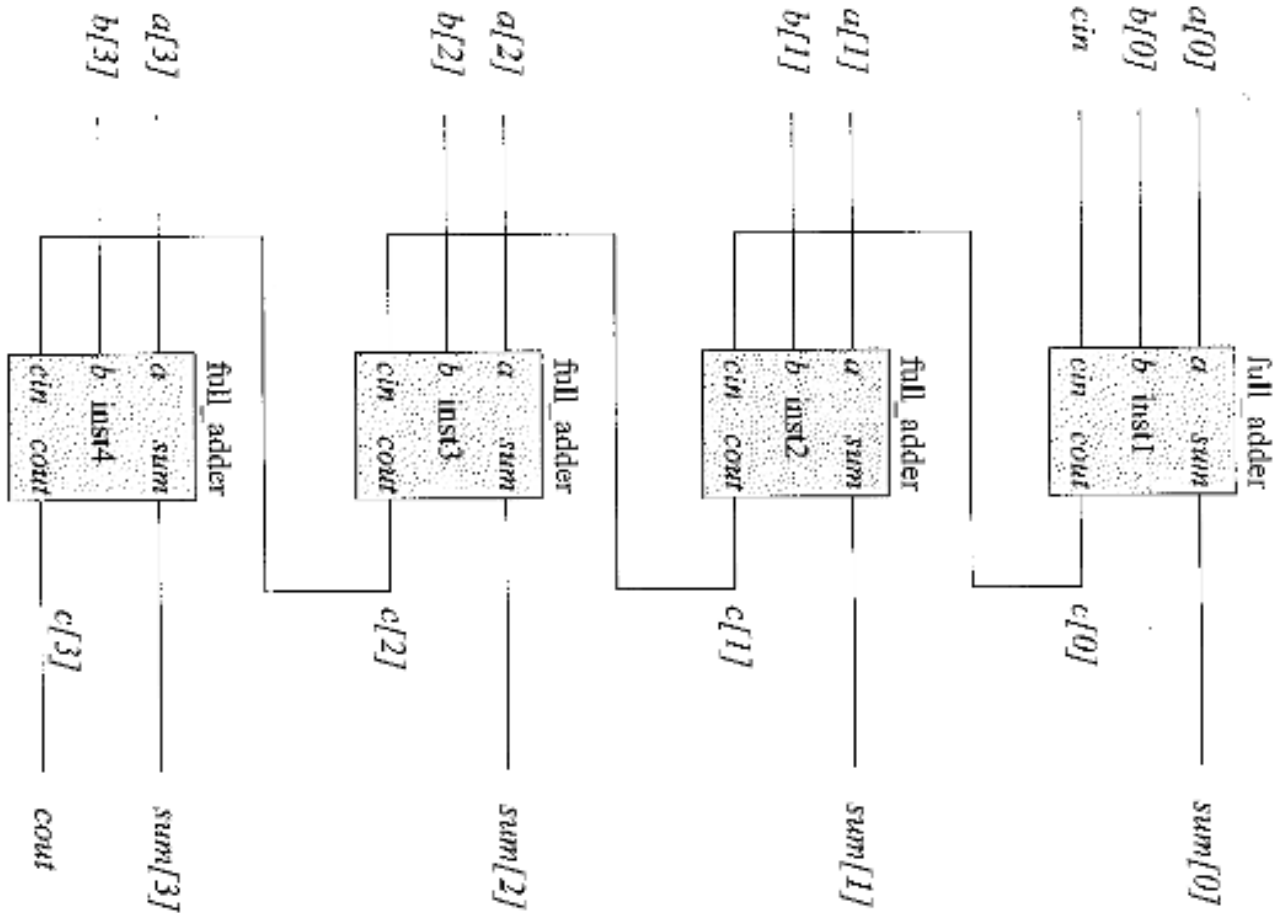
### 3. Structural Modeling (homework?...)

Design a four-bit ripple adder circuit using structural modeling



# Group discussion

---




## 4. Mixed-design Modeling

---

- Incorporates different modeling styles in the same module
- Includes gate, module instantiations, continuous assignment and behavioral constructs
- For example, a full adder can be designed using built-in primitives, dataflow and behavioral modeling

# 4. Mixed-design Modeling

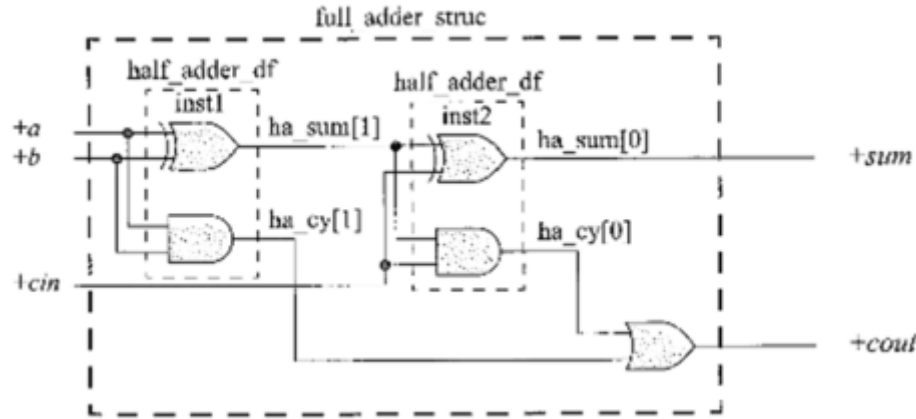

```
//mixed-designed full adder
```

```
Module full_adder_mix
(a,b,cin,sum,cout);
```

```
// list inputs and outputs
```

```
Input a, b, cin;
```

```
Output sum, cout;
```

```
// define reg and wire
```

```
Reg cout;
```

```
Wire a, b, cin;
```

```
Wire sum;
```

```
Wire net1;
```

```
//built-in primitive
```

```
Xor (net1, a,b);
```

```
//behavioral
```

```
Always @ (a or b or cin)
```

```
Begin
```

```
 cout=cin & (a^b)|(a&b);
```

```
End
```

```
//dataflow
```

```
Assign sum=net1^cin;
```

```
endmodule
```

# Exercise & Discussion

---

- Finite state machine (FSM)

