

1 - 1010 SEQUENCE DETECTOR MEALY WITHOUT OVERLAP

```
module melfsm(din, reset, clk, y);
input din;
input clk;
input reset;
output reg y;
reg [1:0] cst, nst;
parameter S0 = 2'b00, //all state
          S1 = 2'b01,
          S2 = 2'b10,
          S3 = 2'b11;
always @(cst or din)
begin
case (cst)
S0: if (din == 1'b1)
begin
nst = S1;
y=1'b0;
end
else
begin
nst = cst;
y=1'b0;
end
S1: if (din == 1'b0)
begin
nst = S2;
y=1'b0;
end
else
begin
nst = cst;
end
S2: if (din == 1'b1)
begin
nst = S3;
y=1'b0;
end
else
begin
nst = S0;
y=1'b0;
end
S3: if (din == 1'b0)
begin
nst = S0;
y=1'b1;
//output will come
end
else
begin
nst = S1;
y=1'b0;
end
default: nst = S0;
endcase
end
always@(posedge clk)
begin
if (reset)
cst <= S0;
else
cst <= nst;
end
endmodule
```

2 - up down counter

```
7 module up_down_counter    (  
8   out      , // Output of the counter  
9   up_down  , // up_down control for counter  
10  clk      , // clock input  
11  data     , // Data to load  
12  reset    , // reset input  
13 );  
14 //-----Output Ports-----  
15 output [7:0] out;  
  
16 //-----Input Ports-----  
17 input [7:0] data;  
18 input up_down, clk, reset;  
  
19 //-----Internal Variables-----  
20 reg [7:0] out;  
  
21 //-----Code Starts Here-----  
22 always @(posedge clk)  
23 if (reset) begin // active high reset  
24   out <= 8'b0 ;  
25 end else if (up_down) begin  
26   out <= out + 1;  
27 end else begin  
28   out <= out - 1;  
29 end  
30  
31 endmodule
```

3 - Vending Machine

```

module vending_moore(N, D, clk, reset, open);
// Moore FSM for a vending machine
input N, D, clk, reset;
output open;
reg [1:0] state;
parameter S0=2'b00, S5=2'b01, S10=2'b10,
S15=2'b11;


```

Synthesizing Moore FSM directly from state diagram

```

// Define the sequential block
always @(posedge reset or posedge clk)
if (reset) state <= S0;
else
  case (state)
    S0: if (N) state <= S5;
        else if (D) state <= S10;
        else state <= S0;
    S5: if (N) state <= S10;
        else if (D) state <= S15;
        else state <= S5;
    S10: if (N) state <= S15;
        else if (D) state <= S15;
        else state <= S10;
    S15: state <= S15;
  endcase
// Define output during S3
assign open = (state == S15);
endmodule

```

 

```

module vending_mealy(N, D, clk, reset, open);
// Mealy FSM for a vending machine
input N, D, clk, reset;
output open;
reg [1:0] pstate, nstate;
reg open;
parameter S0=2'b00, S5=2'b01, S10=2'b10, S15=2'b11;

```

Synthesizing Mealy FSM directly from state diagram

```

// Next state and output combinational logic
always @(N or D or pstate or reset)
if (reset)
  begin nstate = S0; open = 0; end
else case (pstate)
  S0: begin open = 0; if (N) nstate = S5;
        else if (D) nstate = S10;
        else nstate = S0; end
  S5: begin open = 0; if (N) nstate = S10;
        else if (D) nstate = S15;
        else nstate = S5; end
  S10: if (N | D) begin nstate = S15; open = 0; end
        else begin nstate = S10; open = 0; end
  S15: begin nstate = S0; open = 1; end
endcase
// FF logic, use nonblocking assignments "<="
always @(posedge clk)
  pstate <= nstate;
endmodule

```

